

CONCEPTUAL PHYSICS

CH 35 #19-24

4B-5B

KEY

KEY  
4/28/10  
CONC. PHYS  
Per X  
CKTS #3  
1

19.  $R_{eq} = R_1 + R_2$   
 $= 6\Omega + 6\Omega$

$R_{eq} = 12\Omega$

20.  $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$   
 $= \frac{1}{6\Omega} + \frac{1}{6\Omega}$   
 $= \frac{2}{6\Omega}$

$\frac{1}{R_{eq}} = \frac{1}{3\Omega}$

$R_{eq} = 3\Omega$

OR  $R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$   
 $= \frac{(6\Omega)(6\Omega)}{6\Omega + 6\Omega}$   
 $= \frac{36\Omega^2}{12\Omega}$

$R_{eq} = 3\Omega$

21.  $V = IR; I = V/R$   
 $I = \frac{12V}{30\Omega}$

$I = 0.4A$




22.  $R_{eq} = R_1 + R_2 + R_3$   
 $= 30\Omega + 30\Omega + 30\Omega$

$R_{eq} = 90\Omega$

$V = IR_{eq}; I = \frac{V}{R_{eq}}$   
 $I = \frac{12V}{90\Omega}$

$I = 0.13A$


$I = 0.13A$

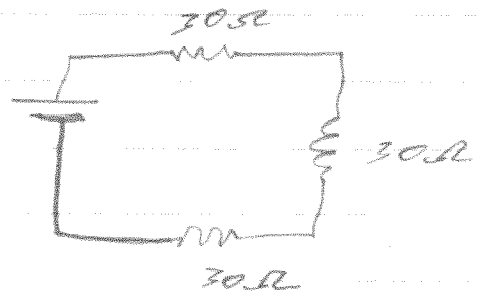

23.  $R_{eq} = R_1 + R_2$

$R_{eq} = 30\Omega + 30\Omega = 48V$

$R_{eq} = 60\Omega$

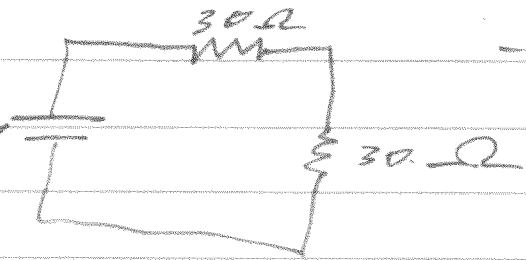

- 2 -

$V = IR; I = \frac{V}{R}$

$I = \frac{48V}{60\Omega}$

$I = 0.8A$

24.  $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$

$\frac{1}{R_{eq}} = \frac{1}{30\Omega} + \frac{1}{30\Omega}$

$= \frac{2}{30\Omega}$

$\frac{1}{R_{eq}} = \frac{1}{15\Omega}$

$R_{eq} = 15\Omega$

$V = IR; I = \frac{V}{R}$

$I = \frac{48V}{15\Omega}$


$I = 3.2A$



48.  $V = IR; I = \frac{V}{R}$


$I = \frac{240V}{30\Omega}$

$I = 8.0A$

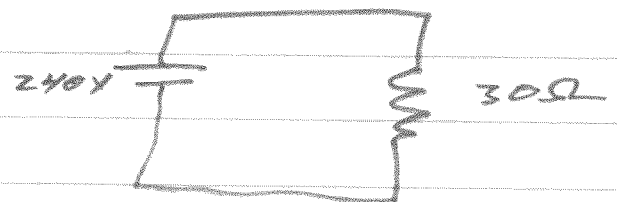


Key  
4/28/10  
Conn. Phy.  
Pet X...  
- 3 -

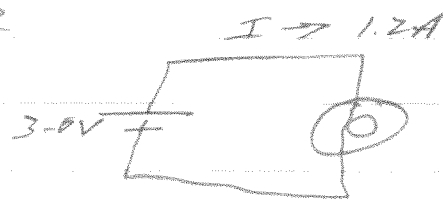49.  $V = IR; \frac{V}{I} = R$   
 $\frac{3.0V}{1.2A} = 2.5\Omega$



$R = 2.5\Omega$

50.  $V = IR$   
 $V = (1.5A)(4\Omega)$

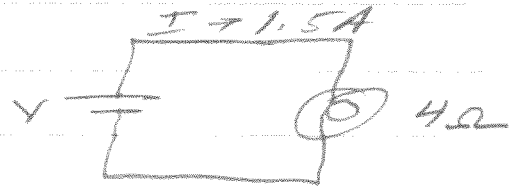

$V = 6.0V$

51.  $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$

$\frac{1}{R_{eq}} = \frac{1}{16\Omega} + \frac{1}{8\Omega}$   
 $= \frac{1}{16\Omega} + \frac{2}{16\Omega}$

$\frac{1}{R_{eq}} = \frac{3}{16\Omega}$

$R_{eq} = \frac{16}{3}\Omega$


$R_{eq} = 5.33\Omega$



52. a. // is 2 10Ω resistors

$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$   
 $= \frac{(10\Omega)(10\Omega)}{10\Omega + 10\Omega}$

$R_{eq} = 5\Omega$

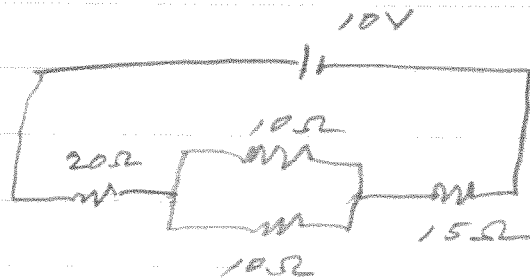

b.  $R_{eq} = R_1 + R_2 + R_3$   
 $R_{eq} = 15\Omega + 5\Omega + 20\Omega$

$R_{eq} = 40\Omega$

53. How many  $4\Omega$  resistors  
in  $\parallel = .5\Omega$  Req?

-4-

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \dots + \frac{1}{R_n}$$

$$\frac{1}{.5\Omega} = n \left( \frac{1}{4\Omega} \right)$$

$$20 = \frac{n}{4\Omega}$$

$$20 \cdot 4\Omega = n$$

$$\boxed{80 = n}$$

54.

Find Req

$$\frac{1}{R_{eq1}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{eq1}} = \frac{1}{20\Omega} + \frac{1}{30\Omega}$$

$$R_{eq1} = \frac{2}{3}\Omega$$

$$\rightarrow R_{eq1} = 15\Omega$$

$$R_{eq2} = R_{eq1} + 5\Omega$$


$$= 15\Omega + 5\Omega$$

$$R_{eq2} = 20\Omega$$

$$V = IR; I = \frac{V}{R}$$


$$I = \frac{10V}{20\Omega}$$

$$\boxed{I = 0.5A}$$

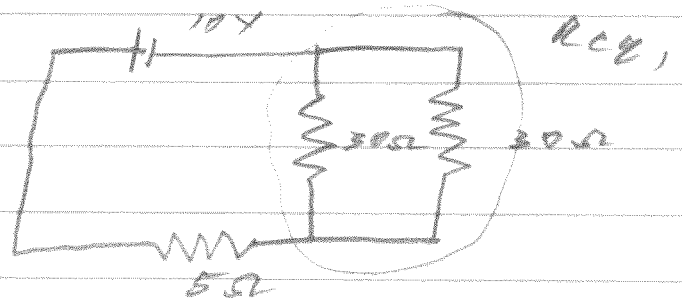

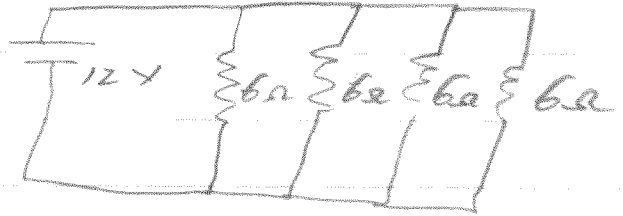55.

$$\begin{aligned}
 a. \quad \frac{1}{R_{eq}} &= \frac{1}{R_1} + \dots + \frac{1}{R_n} \\
 \frac{1}{R_{eq}} &= 4 \left( \frac{1}{6\Omega} \right) \\
 R_{eq} &= 1.5 \Omega
 \end{aligned}$$



$$\begin{aligned}
 b. \quad V &= IR; \quad I = \frac{V}{R} \\
 I &= \frac{12V}{1.5\Omega} \\
 I &= 8.0 \text{ A}
 \end{aligned}$$

56. 4-w bulb; 30 day month  
120V outlet

$$\begin{aligned}
 a. \quad P &= IV; \quad I = \frac{P}{V} \\
 I &= \frac{4W}{120V} \\
 I &= .03 \text{ A or } 30 \text{ mA}
 \end{aligned}$$

$$\begin{aligned}
 b. \quad V &= IR; \quad R = \frac{V}{I} \\
 R &= \frac{120V}{.03 \text{ A}} \\
 R &= 4 \text{ k}\Omega \text{ or } 4 \text{ k}\Omega
 \end{aligned}$$


c. Energy in month

$$4 \text{ W} \cdot \frac{1 \text{ kW}}{1000 \text{ W}} \cdot 30 \text{ d} \cdot \frac{24 \text{ hr}}{1 \text{ d}} = 2.88 \text{ kWh}$$

$$\begin{aligned}
 d. \quad \text{cost} &= r \cdot t \\
 &= \frac{\$}{\text{kWh}} \cdot 2.88 \text{ kWh}
 \end{aligned}$$

$$\text{Cost} = \$ .29$$

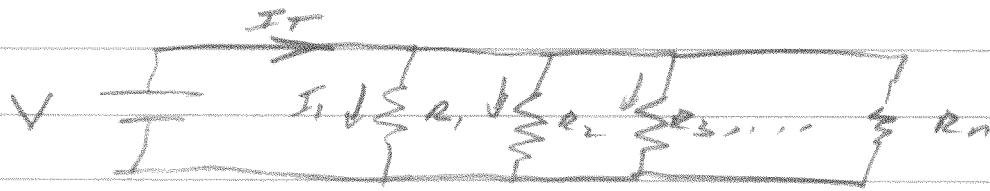57. Prove  $\frac{1}{R_{eq}} = \frac{1}{R_1} + \dots + \frac{1}{R_n}$



$$I_T = \sum_1^n I_n \quad (I_1 + I_2 + \dots + I_n)$$

$$I_n = \frac{V}{R_n} \quad // \text{ Voltage is same}$$

$$I_T = \sum_1^n \frac{V}{R_n} \quad \left( \frac{V}{R_1} + \frac{V}{R_2} + \dots + \frac{V}{R_n} \right)$$

$$I_T = V \left( \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} \right)$$

$$I_T = \frac{V}{R_{eq}} \quad (V = I R)$$

$$\frac{V}{R_{eq}} = V \left( \frac{1}{R_1} + \dots + \frac{1}{R_n} \right)$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

Key  
4/28/10  
conc. Phy  
Per X

5B. slow Req



$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{eq}} = \frac{R_2}{R_1 R_2} + \frac{R_1}{R_1 R_2}$$

Common Denominator

$$\frac{1}{R_{eq}} = \frac{R_1 + R_2}{R_1 R_2}$$

Simplify

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

Invert